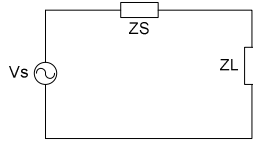


Maximum Power Transfer

Consider the following circuit: The input voltage is sinusoidal with a peak value V_s . The source impedance is $Z_s = R_s + jX_s$ and the load impedance is $Z_L = R_L + jX_L$.



The magnitude of the current flowing in the circuit is:

$$I = \frac{V_s}{|Z_s + Z_L|}$$

The power dissipated by the load is:

$$P_L = I_{rms}^2 R_L = \frac{V_s^2 R_L}{2|Z_s + Z_L|^2} = \frac{V_s^2 R_L}{2[(R_s + R_L)^2 + (X_s + X_L)^2]}$$

If we want to find the load that maximizes the above power, we have to solve the equations:

$$\nabla P_L = 0 \text{ or the system of equations: } \begin{cases} \frac{\partial P_L}{\partial R_L} = 0 \\ \frac{\partial P_L}{\partial X_L} = 0 \end{cases}$$

$$\text{and } \frac{\partial P_L}{\partial X_L} = \frac{V_s^2 R_L (X_s + X_L)}{[(X_s + X_L)^2 + (R_s + R_L)^2]^2}$$

$$\frac{\partial P_L}{\partial R_L} = \frac{V_s^2 [(X_s + X_L)^2 + (R_s + R_L)^2 - 2R_L(R_s + R_L)]}{2[(X_s + X_L)^2 + (R_s + R_L)^2]^2}$$

Setting both equations to zero provides: $X_L = -X_s$ and $R_L = R_s$. In other words: $Z_L = Z_s^*$.

Conclusion:

In order to transfer the maximum of power from a source, the load must be matched: The load reactance should cancel the source reactance and the load resistance must be equal to the source one.